

Tutorial exercises No 7

Exercise 01:

Course Questions

1. Determine the command words (in mode 0) to write into the command register of the 8255A PPI for the following configurations:
 - a) PORTA as input, PORTB as input, and PORTC as output.
 - b) PORTA as output, PORTB as input, and PORTC as input.
 - c) PORTA as input, PORTB as output, PORTC (lower) as output, and PORTC (upper) as input.
2. Determine the states of signals **A1**, **A0**, **RD**, **WR**, and **CS** for:
 - a) Reading from PORTA.
 - b) Writing to the command register (Reg_Com).
3. If the command register contains the value **99H**:

Determine the configuration of the ports (input or output) of the 8255A and the mode being used.

Exercise 02:

Create the flowchart and write an assembly program to display numbers from 0 to 15 on a 7-segment display. Each number is displayed for 1 second (using a 1-second delay). The address of PORTA is **200H**. Mode 0 is used to program the PPI. PORTB and the upper part of PORTC are not connected and must be configured as outputs. The display used is a common anode 7-segment display with 2 digits, multiplexed. The units digit is selected via transistor **Q1**, and the tens digit is selected via transistor **Q2**. A **7447 BCD-to-7-segment decoder** is used to drive the display. See the circuit diagram below.

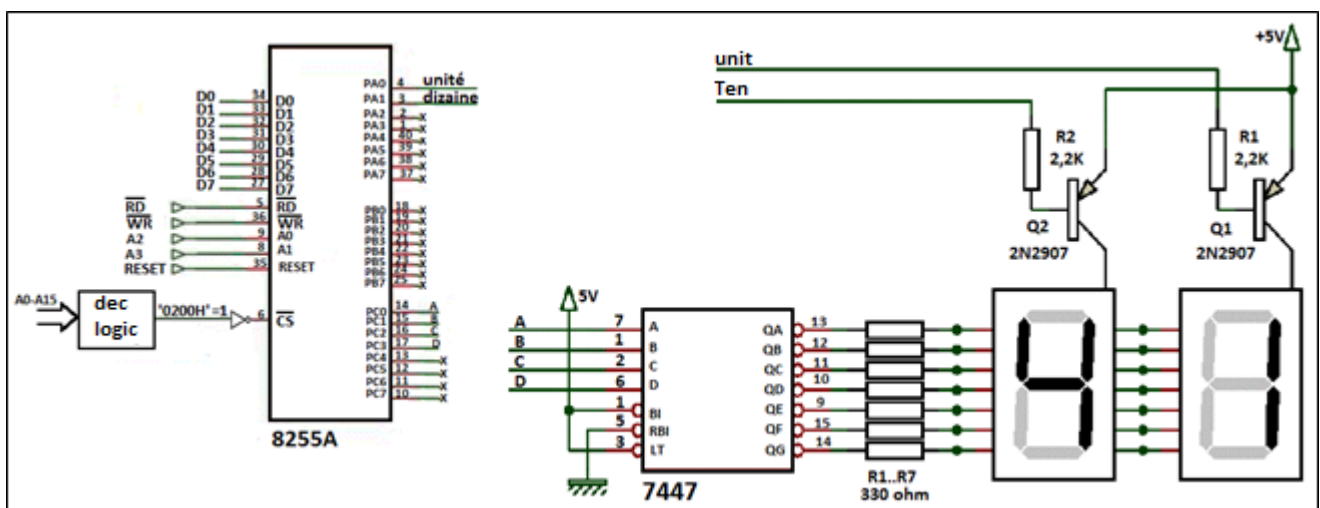


Figure 7.1. Interface Diagram for a 7-Segment Display

Exercise 03:

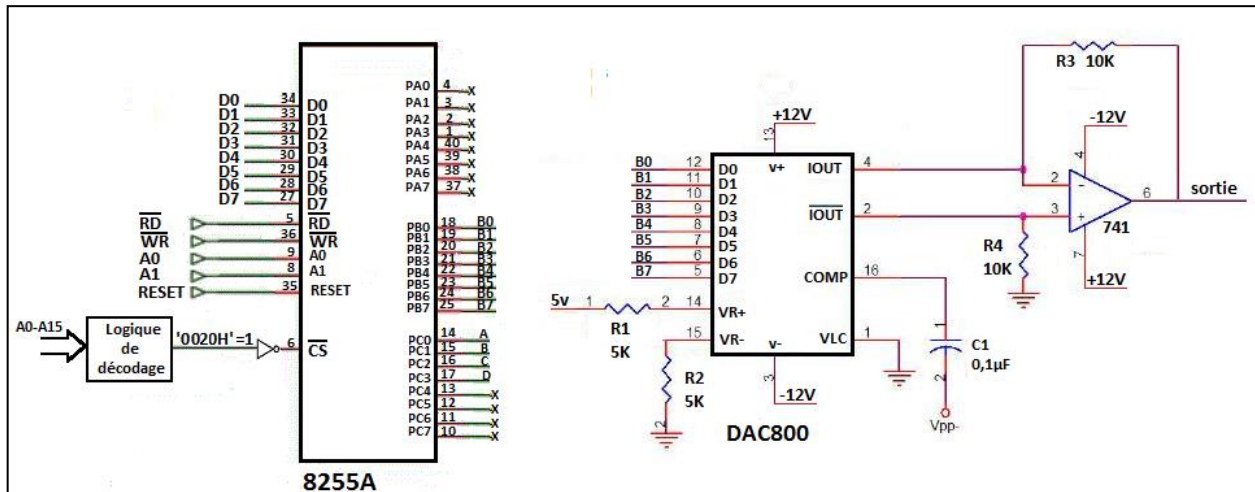


Figure 7.2. Interface Diagram for the Digital-to-Analog Converter DAC800

Create the flowchart and write a program to generate a triangular signal with a period of 60 ms. The main program uses a 0.5 ms delay subroutine (tempo). The ports (**PORTA** and **PORTB**) are not connected and must be configured as outputs. The 8255A is configured in mode 0.

Exercise 04:

In the diagram below, a 16-key keypad is used, organized in a 4x4 matrix of push buttons. A 8255A PPI is used to interface it with the 8086. The lines of **PORTC** are connected to the columns, and the lines of **PORTA** are connected to the rows.

- **PORTC** is configured as output, and **PORTA** as input.
- The 8255 sequentially sets each line of its output to logic "1". If a key is pressed, the corresponding column will then go to logic "1". Knowing which row is at logic "1", the pressed key in the matrix can be identified.

Write a program to identify the pressed key.

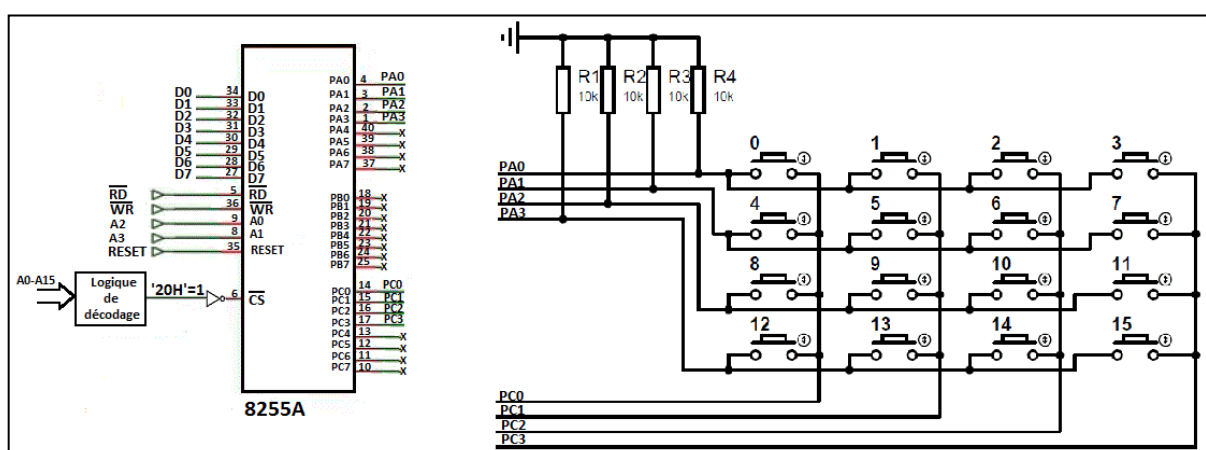


Figure 7.3. Interface Diagram of a 4x4 16-Key Keypad

Exercise 05:

Create the flowchart and write a program to control a two-phase unipolar stepper motor. The motor should rotate in the clockwise direction (operating in full-step mode with maximum torque). (See the figure below.)

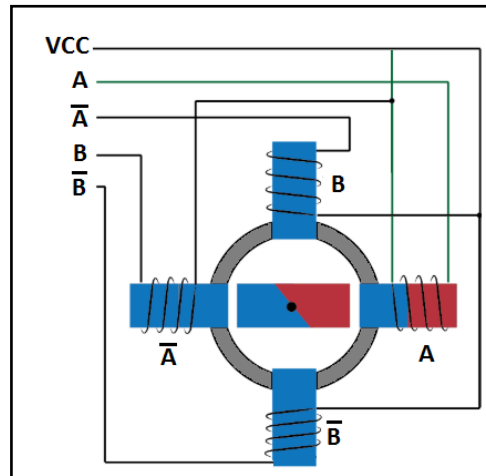


Figure 7.4. Two-Phase Unipolar Stepper Motor

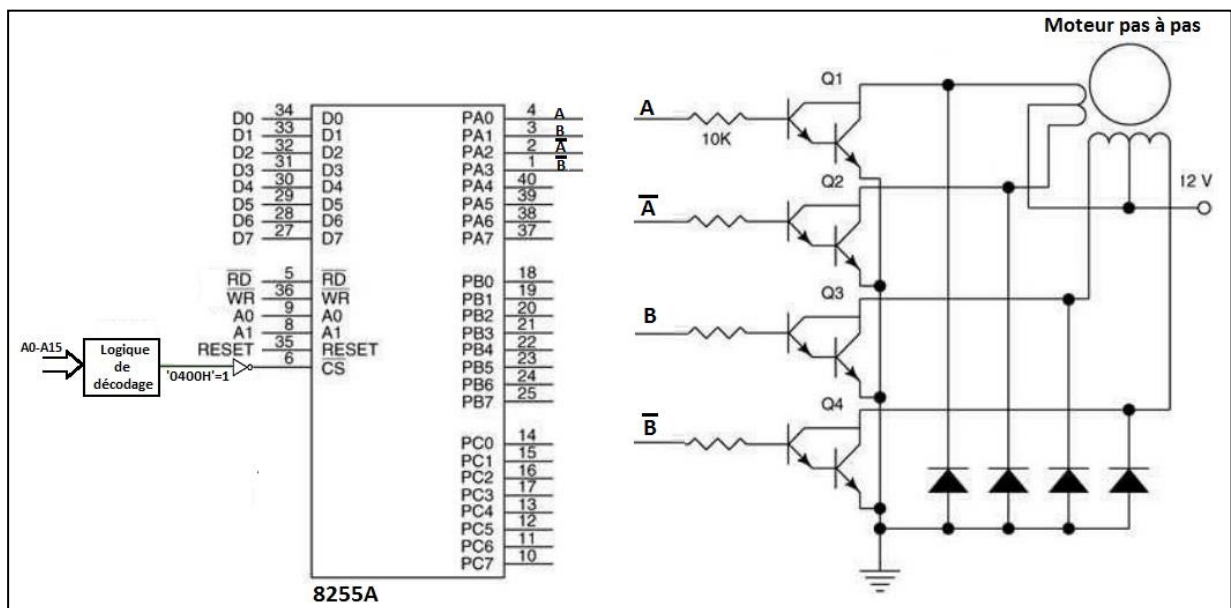


Figure 7.5. Interface Diagram of the Stepper Motor